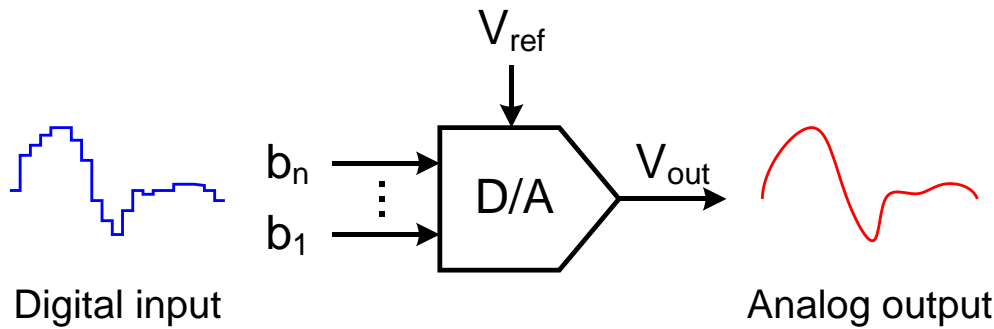


DAC Architectures

Vishal Saxena

Static Performance of DACs

DAC Transfer Characteristics




- $N = \#$ of bits
- $V_{FS} =$ Full-scale range
- $\Delta = V_{FS}/2^N = 1\text{LSB}$
- $b_i = 0$ or 1


$$V_{out} = V_{FS} \cdot \sum_{i=0}^{N-1} \frac{b_i}{2^{N-i}} = \Delta \cdot \sum_{i=0}^{N-1} b_i \cdot 2^{i-N}$$

Note: $V_{out} (b_i = 1, \text{ for all } i) = V_{FS} - \Delta = V_{FS}(1-2^{-N}) \neq V_{FS}$


Ideal DAC Transfer Curve

 


Offset

 


Gain Error

 

Monotonicity

 


Differential and Integral Nonlinearities

 

$$DNL_i = \frac{i^{\text{th}} \text{ Step Size} - \Delta}{\Delta}$$

- DNL = deviation of an output step from 1 LSB ($= \Delta = V_{FS}/2^N$)
- INL = deviation of the output from the ideal transfer curve


DNL and INL

 


$$INL_i = \sum_{j=0}^i DNL_j$$

INL = cumulative sum of DNL

DNL and INL

 


Smooth

 

Noisy


- DNL measures the uniformity of quantization steps, or incremental (local) nonlinearity; small input signals are sensitive to DNL.
- INL measures the overall, or cumulative (global) nonlinearity; large input signals are often sensitive to both INL (HD) and DNL (QE).

Measure DNL and INL (Method I)

 


Endpoints of the transfer characteristic are always at 0 and $V_{FS} - \Delta$

Measure DNL and INL (Method II)

 


Endpoints of the transfer characteristic may not be at 0 and $V_{FS}-\Delta$

Measure DNL and INL

 

Method I (endpoint stretch)

$$\Sigma(INL) \neq 0$$

 

Method II (LS fit & stretch)

$$\Sigma(INL) = 0$$


DAC Architectures

DAC Architecture

- Nyquist DAC architectures
 - Binary-weighted DAC
 - Unit-element (or thermometer-coded) DAC
 - Segmented DAC
 - Resistor-string, current-steering, charge-redistribution DACs
- Oversampling DAC
 - Oversampling performed in digital domain (zero stuffing)
 - Digital noise shaping ($\Sigma\Delta$ modulator)
 - 1-bit DAC can be used
 - Analog reconstruction/smoothing filter


Binary-Weighted DAC

Binary-Weighted CR DAC

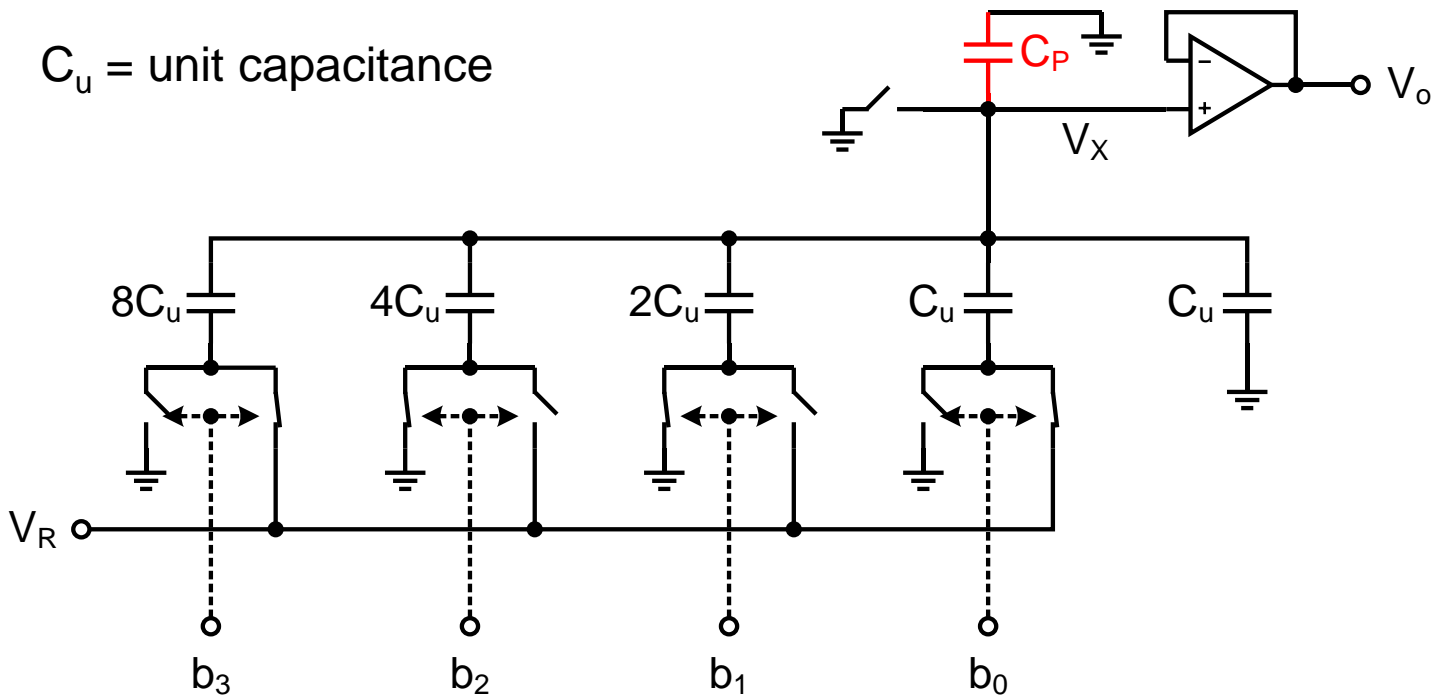

- Binary-weighted capacitor array → most efficient architecture
- Bottom plate @ V_R with $b_j = 1$ and @ GND with $b_j = 0$

Binary-Weighted CR DAC

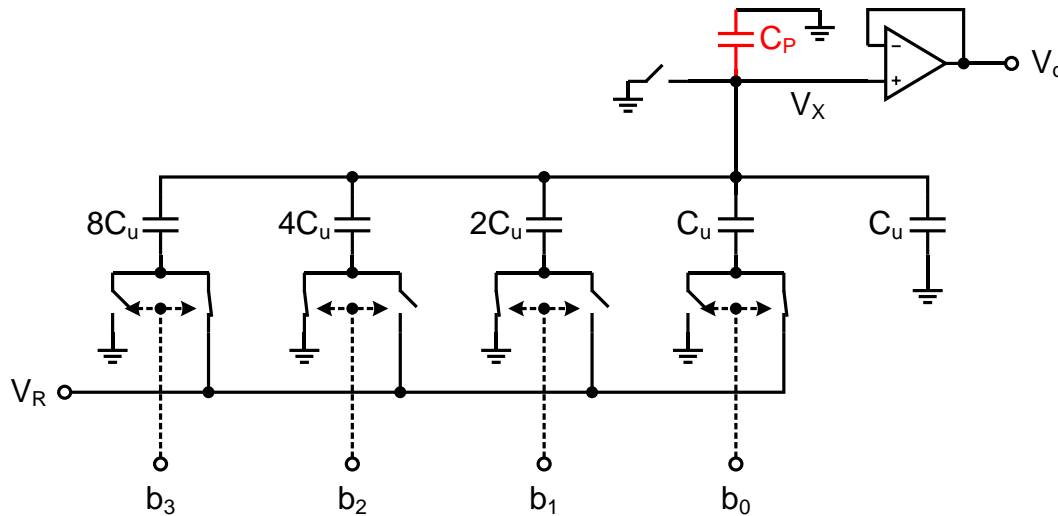

$$V_o = \left(\frac{\sum_{j=1}^N b_{N-j} \cdot 2^{N-j} C_u}{C_p + C_u + \sum_{j=1}^N 2^{N-j} C_u} \right) \cdot V_R$$


$$= \left(\frac{\sum_{j=1}^N b_{N-j} \cdot 2^{N-j} C_u}{C_p + 2^N C_u} \right) \cdot V_R$$

$$V_o = \left(\frac{2^N C_u}{C_p + 2^N C_u} \right) \cdot V_R \cdot \sum_{j=1}^N \frac{b_{N-j}}{2^j}$$

- $C_p \rightarrow$ gain error (nonlinearity if C_p is nonlinear)
- INL and DNL limited by capacitor array mismatch

Stray-Insensitive CR DAC
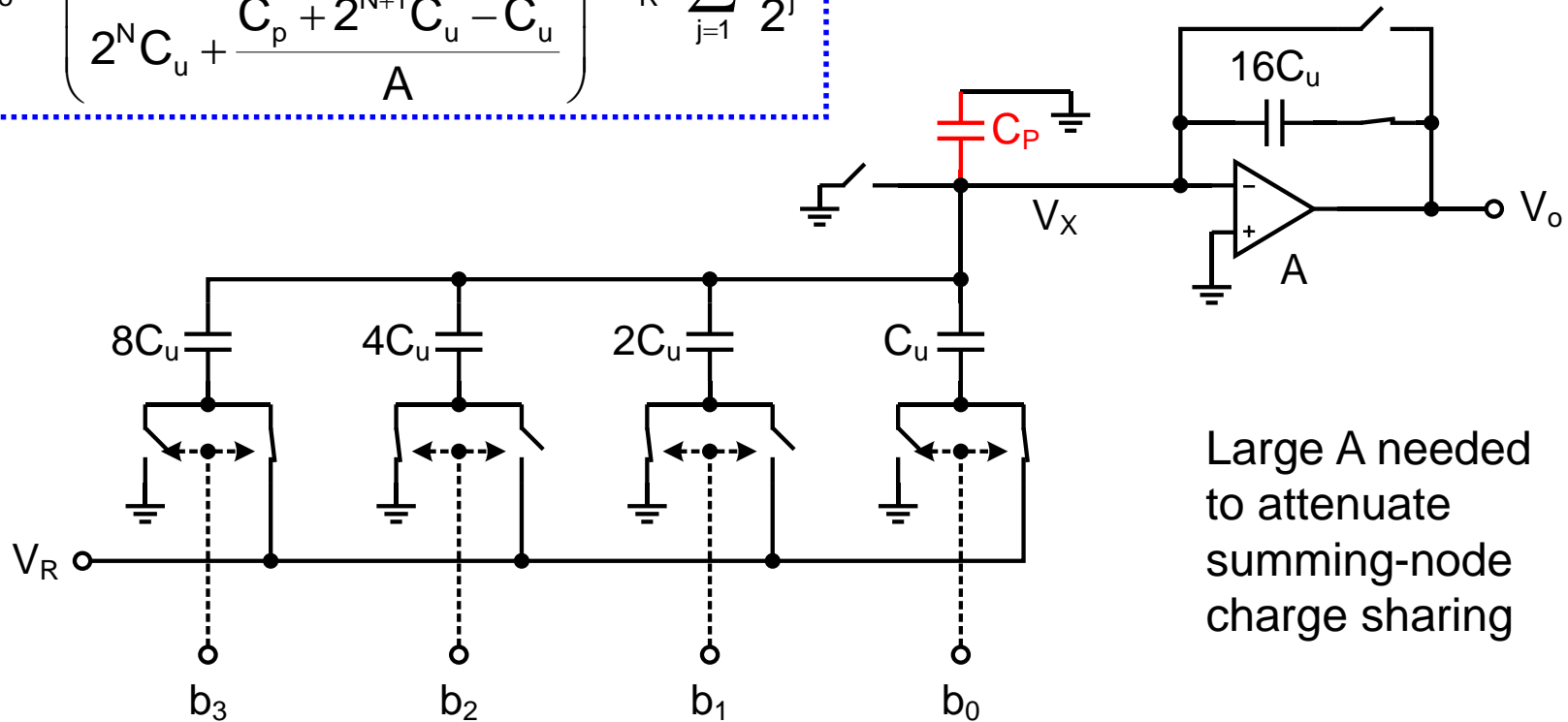
$$V_o = \left(\frac{2^N C_u}{2^N C_u + \frac{C_p + 2^{N+1} C_u - C_u}{A}} \right) \cdot V_R \cdot \sum_{j=1}^N \frac{b_{N-j}}{2^j}$$



Large A needed to attenuate summing-node charge sharing

MSB Transition

Code 0111

$$V_o(0111) = \left(\frac{C_1 + C_2 + C_3}{C_p + C + \sum_{j=1}^4 2^{4-j} C} \right) \cdot V_R$$

Code 1000

$$V_o(1000) = \left(\frac{C_4}{C_p + C + \sum_{j=1}^4 2^{4-j} C} \right) \cdot V_R$$

$$\text{Assume: } C_4 - (C_1 + C_2 + C_3) = C_u + \delta C,$$


$$\text{DNL} = [V_o(1000) - V_o(0111) - 1\text{LSB}] / 1\text{LSB}$$

$$= \frac{\delta C}{\sum C} / \frac{C_u}{\sum C} = \delta C / C_u$$


Largest DNL error occurs at the midpoint where MSB transitions, determined by the mismatch between the MSB capacitor and the rest of the array.

Midpoint DNL

$\delta C > 0$

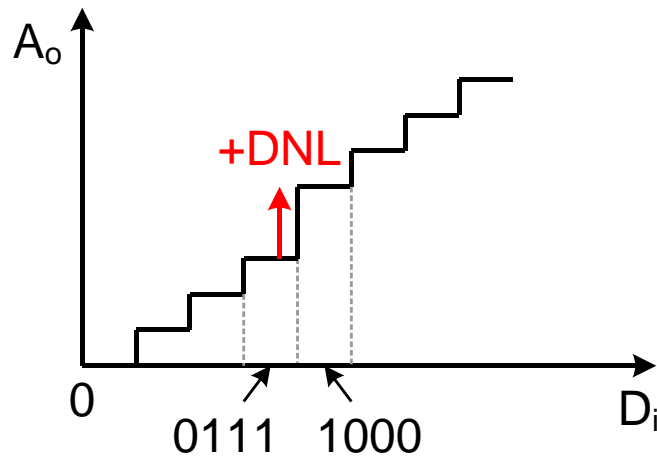


$\delta C < 0$

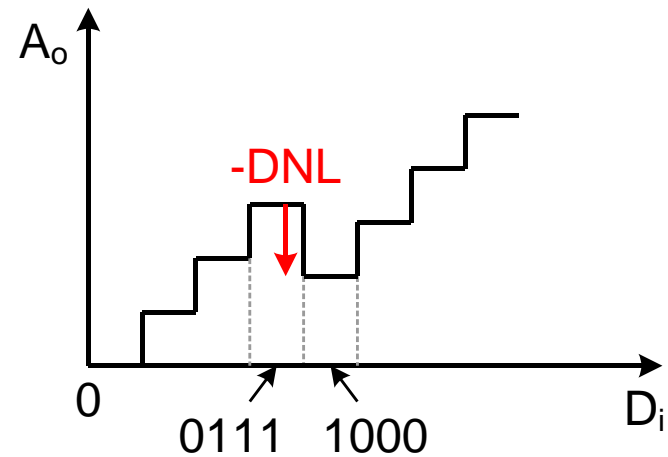

- $\delta C > 0$ results in positive DNL
- $\delta C < 0$ results in negative DNL or even nonmonotonicity


Output Glitches

 


- Cause: Signal and clock skew in circuits
- Especially severe at MSB transition where all bits are switching –
0111...111 →
1000...000

- Glitches cause waveform distortion, spurs and elevated noise floors
- High-speed DAC output is often followed by a de-glitching SHA

De-Glitching SHA

 


 SHA samples the output of the DAC after it settles and then hold it for T , removing the glitching energy.



SHA output must be smooth (exponential settling can be viewed as pulse shaping \rightarrow SHA BW does not have to be excessively large).

Frequency Response

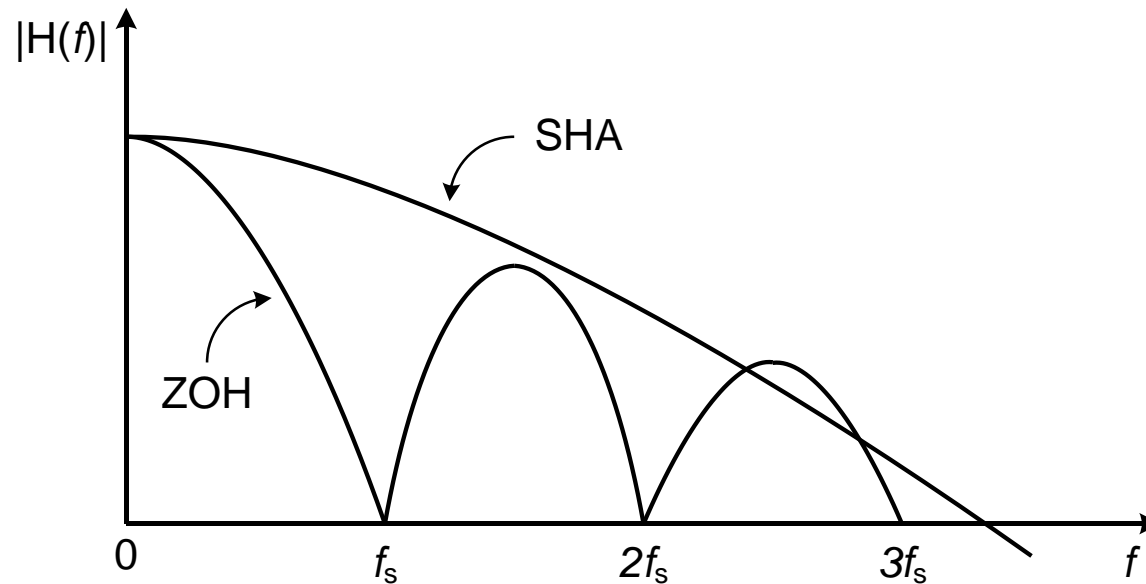


$$H_{\text{ZOH}}(j\omega) = e^{-j\frac{\omega T}{2}} \cdot \frac{\sin(\omega T/2)}{\omega T/2}$$

$$H_{\text{SHA}}(j\omega) = \frac{1}{1 + j\omega/\omega_{-3\text{dB}}}$$

Binary-Weighted Current-Steering DAC

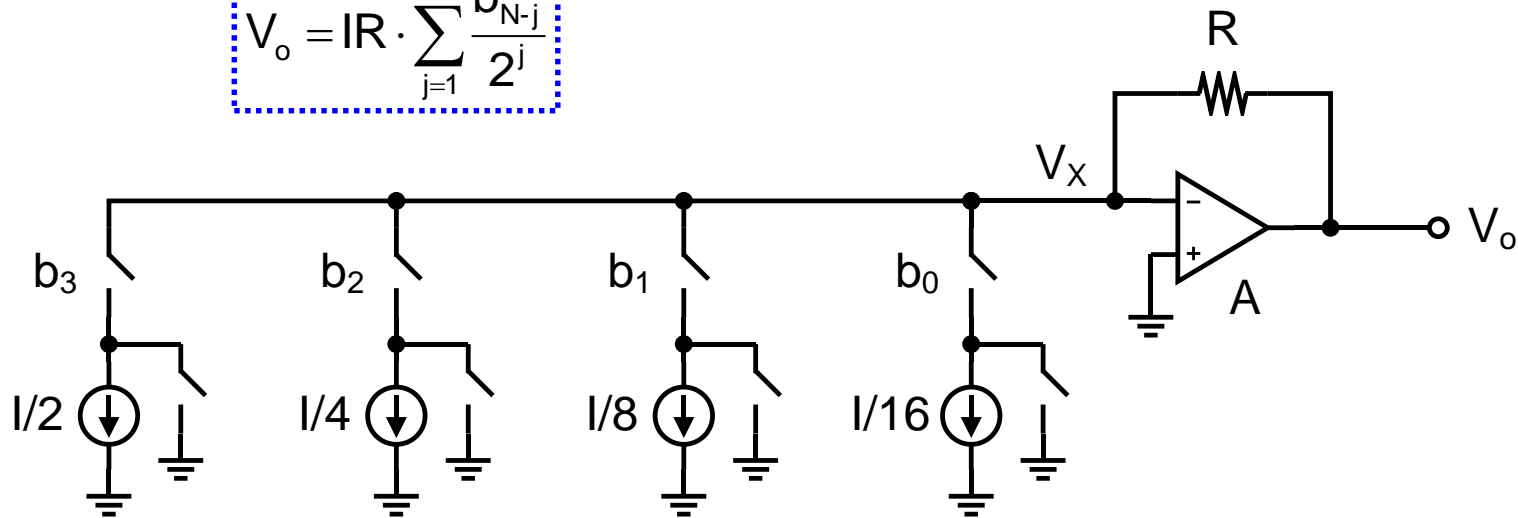
$$V_o = IR \cdot \sum_{j=1}^N \frac{b_{N-j}}{2^j}$$



- Current switching is simple and fast
- V_o depends on R_{out} of current sources without op-amp
- INL and DNL depend on matching, not inherently monotonic
- Large component spread ($2^{N-1}:1$)

R-2R DAC

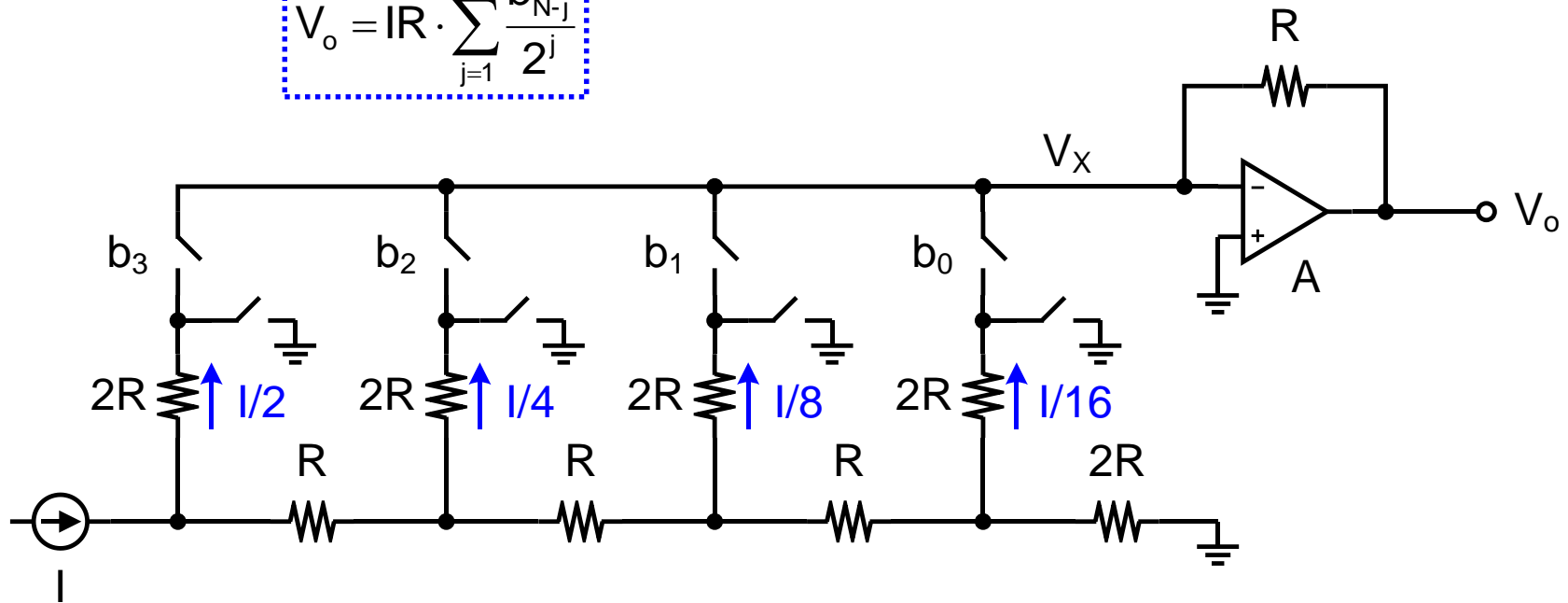
$$V_o = IR \cdot \sum_{j=1}^N \frac{b_{N-j}}{2^j}$$



- A binary-weighted current DAC
- Component spread greatly reduced (2:1)



Unit-Element DAC

Resistor-String DAC

 


- Simple, inherently monotonic \rightarrow good DNL performance
- Complexity \uparrow speed \downarrow for large N , typically $N \leq 8$ bits

Code-Dependent R_o

  

- R_o of ladder varies with signal (code)
- On-resistance of switches depend on tap voltage

DNL

 

$$V_j = \frac{\sum_1^{j-1} R_k}{\sum_1^N R_k} \cdot V_R = \frac{(j-1)R + \sum_1^{j-1} \Delta R_k}{NR + \sum_1^N \Delta R_k} \cdot V_R$$

$$V_{j-1} = \frac{(j-2)R + \sum_1^{j-2} \Delta R_k}{NR + \sum_1^N \Delta R_k} \cdot V_R$$

$$V_j - V_{j-1} = \frac{R + \Delta R_{j-1}}{NR + \sum_1^N \Delta R_k} \cdot V_R \approx \frac{V_R}{N} + \frac{\Delta R_{j-1}}{NR} \cdot V_R$$

$$DNL_j = \left(V_j - V_{j-1} - \frac{V_R}{N} \right) / \frac{V_R}{N} \approx \frac{\Delta R_{j-1}}{R} \Rightarrow \overline{DNL} = 0, \sigma_{DNL} = \frac{\sigma_R}{R}$$

$$V_j = \frac{\sum_{k=1}^{j-1} R_k}{\sum_{k=1}^N R_k} \cdot V_R = \frac{(j-1)R + \sum_{k=1}^{j-1} \Delta R_k}{NR + \sum_{k=1}^N \Delta R_k} \cdot V_R \approx \frac{j-1}{N} V_R + \frac{(N-j+1) \sum_{k=1}^{j-1} \Delta R_k - (j-1) \sum_{k=j}^N \Delta R_k}{N^2 R} V_R$$

$$\Rightarrow \bar{V}_j = \frac{j-1}{N} V_R, \quad \sigma_{V_j}^2 \approx \frac{(j-1)(N-j+1)}{N^3} \frac{\sigma_R^2}{R^2} V_R^2$$

$$\Rightarrow \sigma_{V_j}^2(\max) \approx \frac{1}{4N} \frac{\sigma_R^2}{R^2} V_R^2, \quad \text{when } j = \frac{N}{2} + 1 \approx \frac{N}{2}$$


$$\text{INL}_j = \left(V_j - \frac{j-1}{N} V_R \right) / \frac{V_R}{N} \Rightarrow \overline{\text{INL}} = 0, \quad \sigma_{\text{INL}}(\max) \approx \frac{\sqrt{N}}{2} \left(\frac{\sigma_R}{R} \right)$$

INL and DNL of Binary-Wtd DAC

A Binary Weighted DAC is typically constructed using unit elements, the same way as that of a Unit Element DAC, for good component matching accuracy.


$$\begin{aligned} \Rightarrow \quad \overline{\text{INL}} &= 0, \quad \sigma_{\text{INL}}(\text{max}) \approx \frac{\sqrt{N}}{2} \left(\frac{\sigma_R}{R} \right) \\ \overline{\text{DNL}} &= 0, \quad \sigma_{\text{DNL}}(\text{max}) = 2 \cdot \text{INL} \approx \sqrt{N} \left(\frac{\sigma_R}{R} \right) \end{aligned}$$

Current-Steering DAC

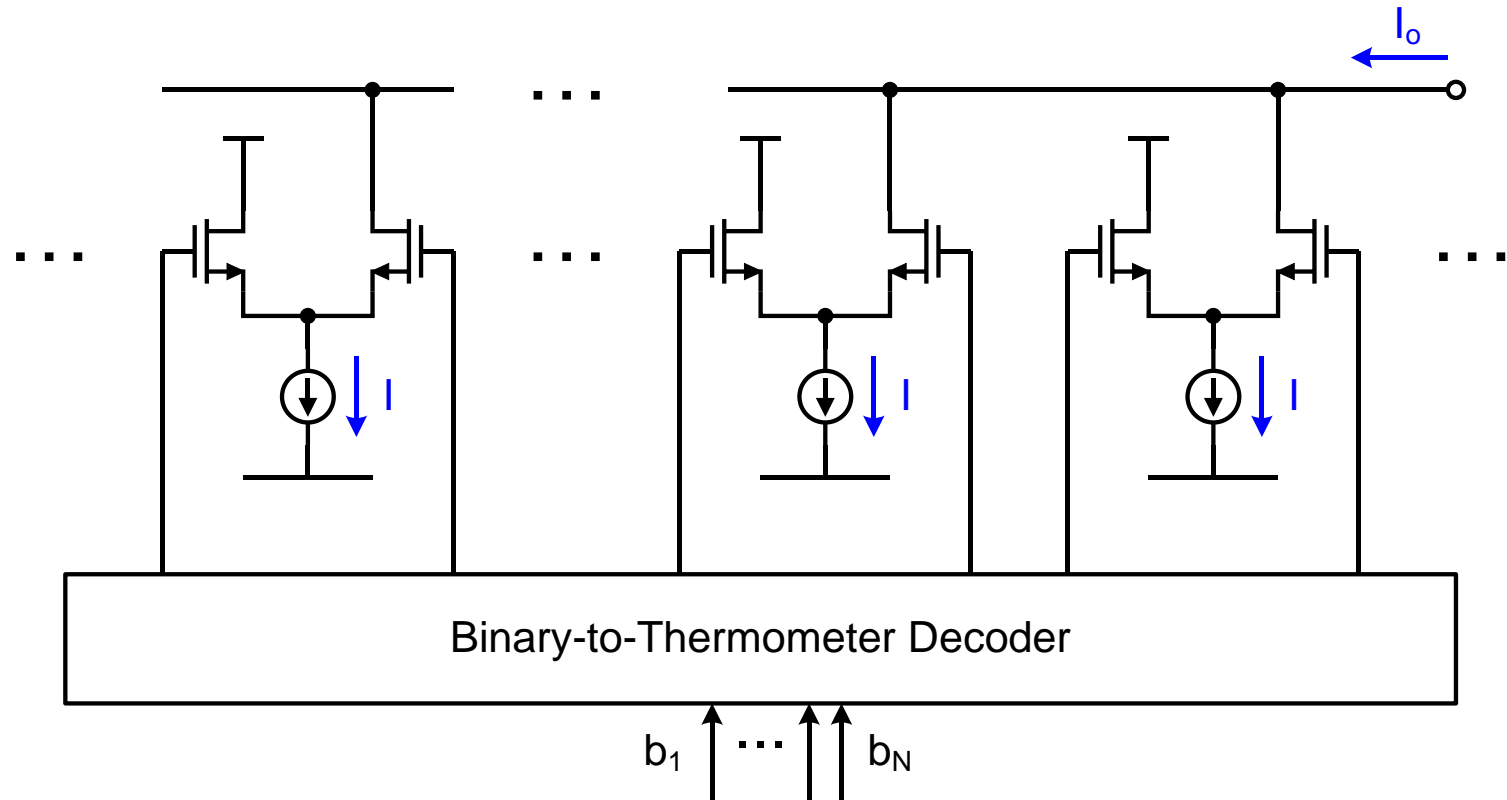

- Fast, inherently monotonic \rightarrow good DNL performance
- Complexity increases for large N , requires B2T decoder

Unit Current Cell

 

- 2^N current cells typically decomposed into a $(2^{N/2} \times 2^{N/2})$ matrix
- Current source cascoded to improve accuracy (R_o effect)
- Coupled inverters improve synchronization of current switches

Segmented DAC

BW vs. UE DACs

Binary-weighted DAC


- Pros
 - Min. # of switched elements
 - Simple and fast
 - Compact and efficient
- Cons
 - Large DNL and glitches
 - Monotonicity not guaranteed
- INL/DNL
 - $\text{INL}(\text{max}) \approx (\sqrt{N}/2)\sigma$
 - $\text{DNL}(\text{max}) \approx 2 \cdot \text{INL}$

Unit-element DAC

- Pros
 - Good DNL, small glitches
 - Linear glitch energy
 - Guaranteed monotonic
- Cons
 - Needs B2T decoder
 - complex for $N \geq 8$
- INL/DNL
 - $\text{INL}(\text{max}) \approx (\sqrt{N}/2)\sigma$
 - $\text{DNL}(\text{max}) \approx \sigma$

Combine BW and UE architectures → Segmentation

Segmented DAC

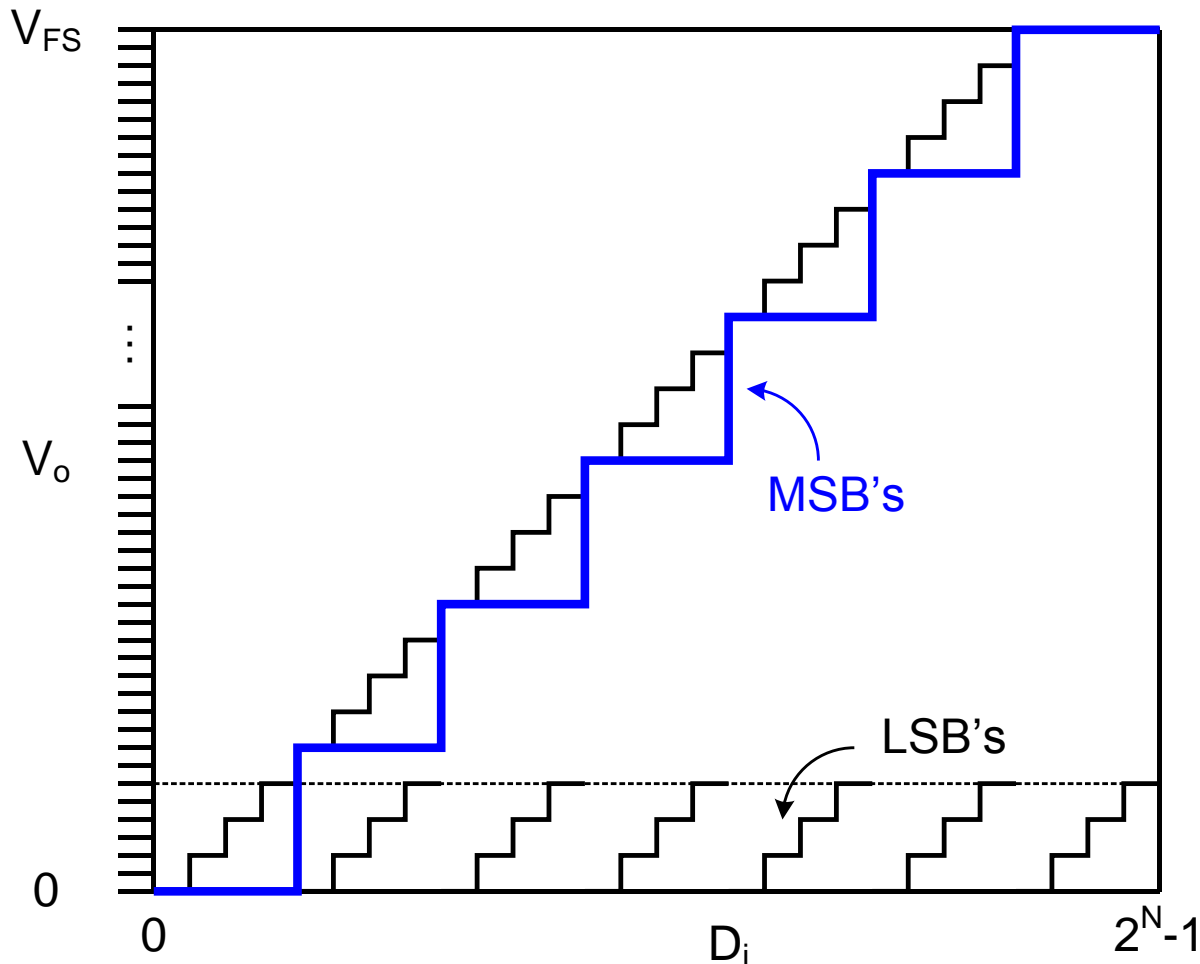

- MSB DAC: M-bit UE DAC
- LSB DAC: L-bit BW DAC
- Resolution: $N = M + L$
- $2^M + L$ switching elements
- Good DNL
- Small glitches
- Same INL as BW or UE


Comparison

Example: $N = 12$, $M = 8$, $L = 4$, $\sigma = 1\%$

Architecture	σ_{INL}	σ_{DNL}	# of s.e.
Unit-element	0.32 LSB's	0.01 LSB's	$2^N = 4096$
Binary-weighted	0.32 LSB's	0.64 LSB's	$N = 12$
Segmented	0.32 LSB's	0.06 LSB's	$2^{M+L} = 260$


Max. DNL error occurs at the transitions of MSB segments

Example: "8+2" Segmented Current DAC

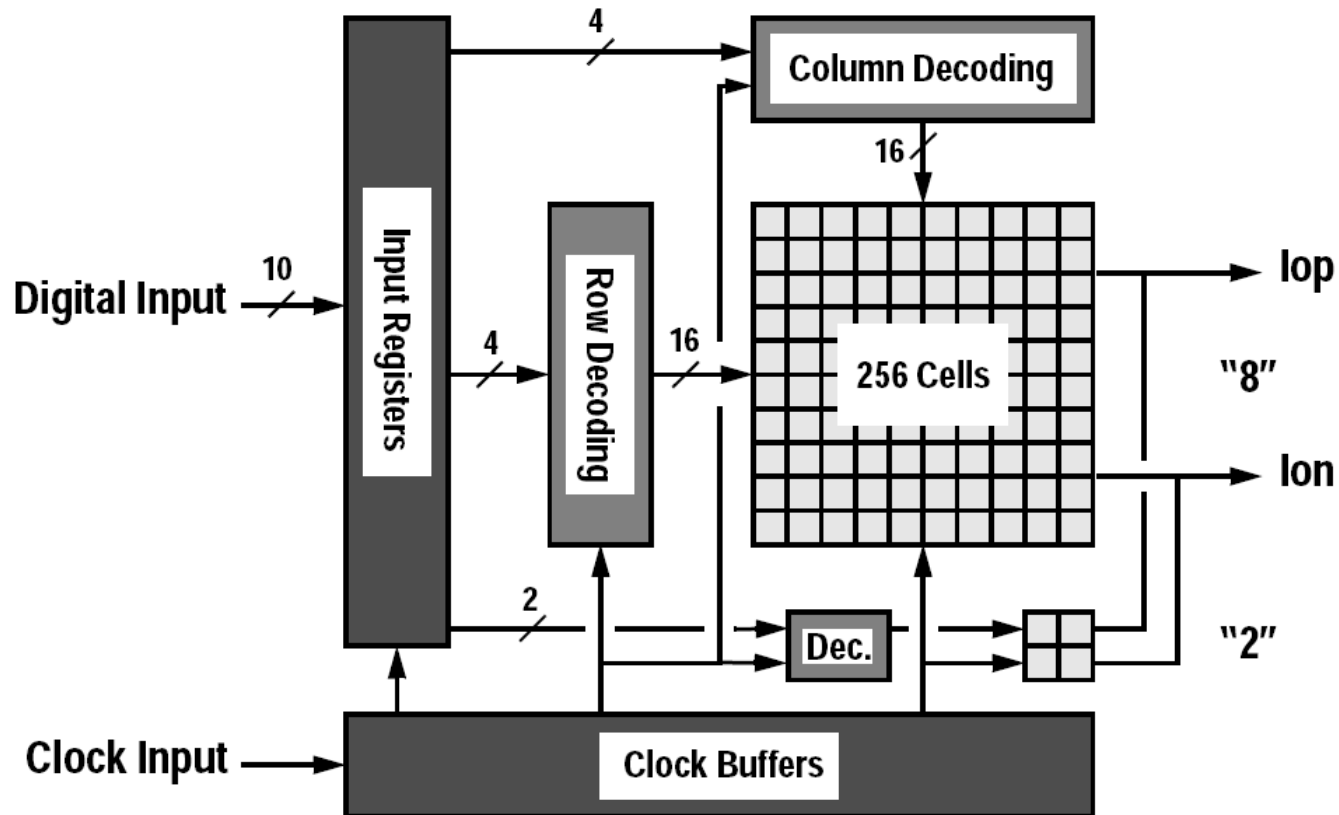

Ref: C.-H. Lin and K. Bult, "A 10-b, 500-MSample/s CMOS DAC in 0.6mm²," *IEEE Journal of Solid-State Circuits*, vol. 33, pp. 1948-1958, issue 12, 1998.


MSB-DAC Biasing Scheme

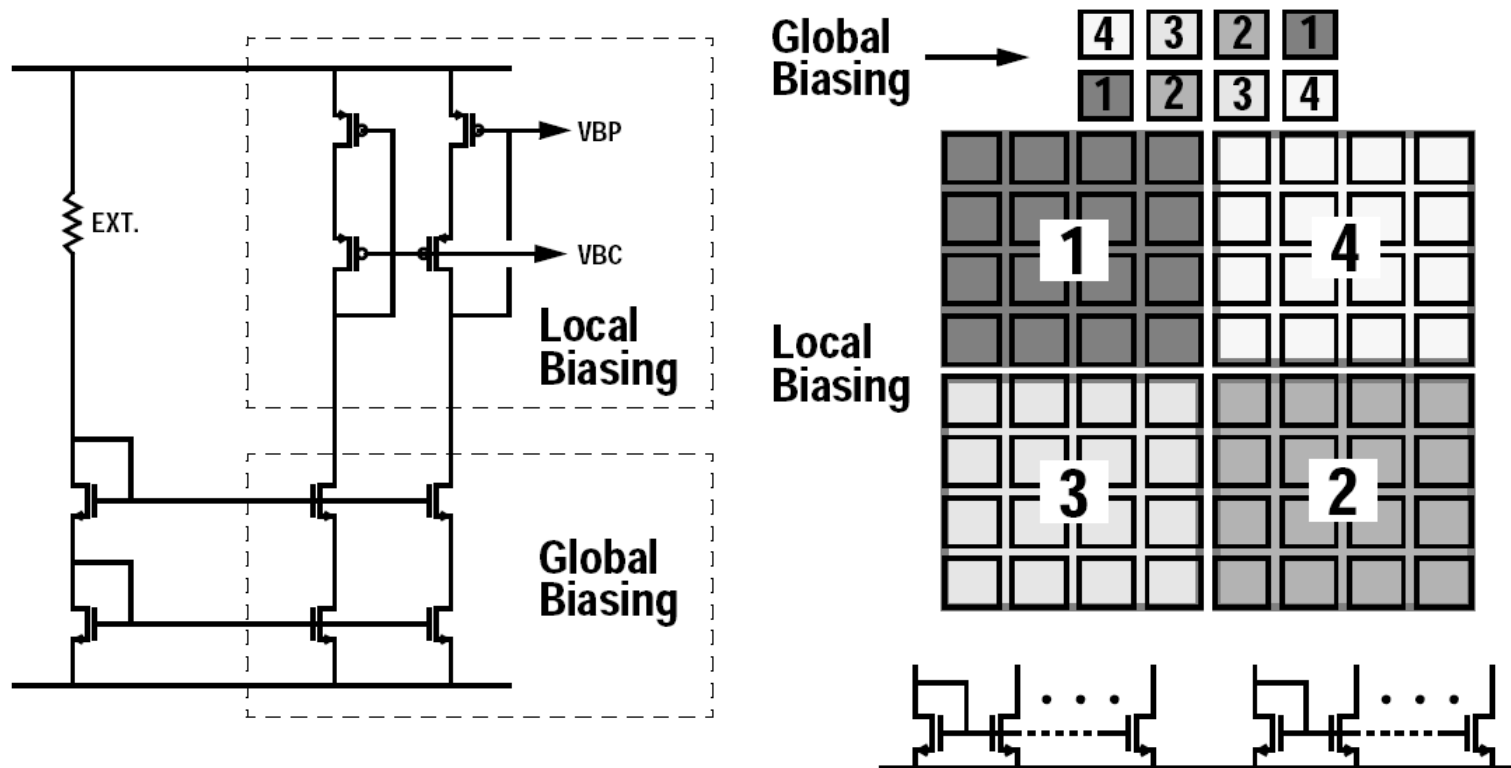



Common-centroid global biasing + divided 4 quadrants of current cells

MSB-DAC Biasing Scheme


Chip A: Merged 4 quadrants

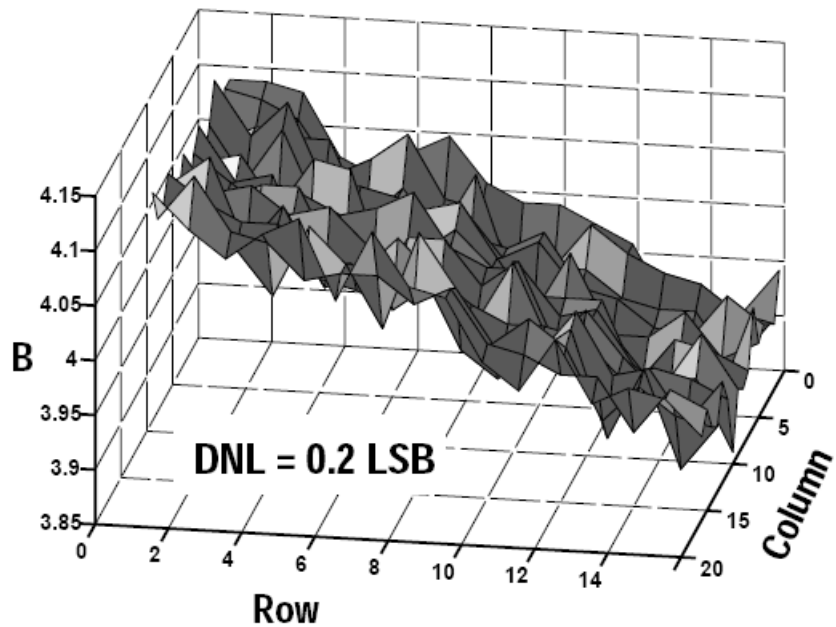


Chip B: Separated 4 quadrants

 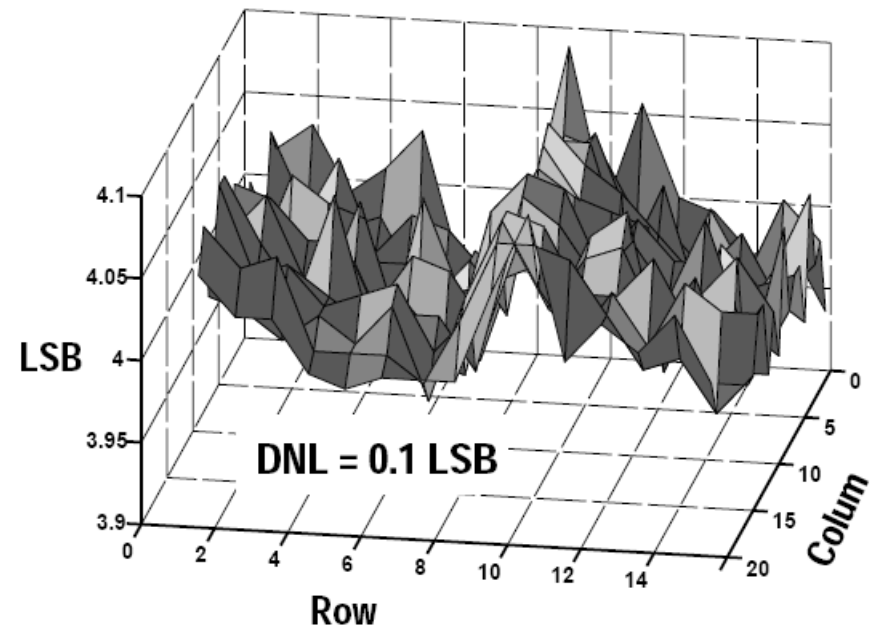

Randomization and Dummies


 


 - Column and row randomization to improve INL



■ Dummy-cell □ Active-cell

Current-Steering DAC Calibration

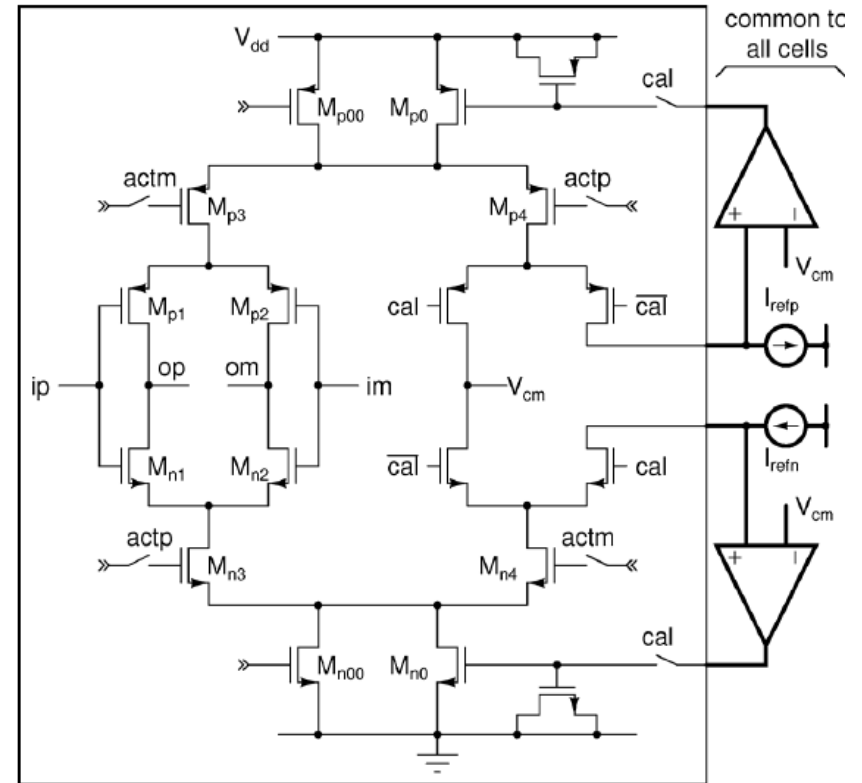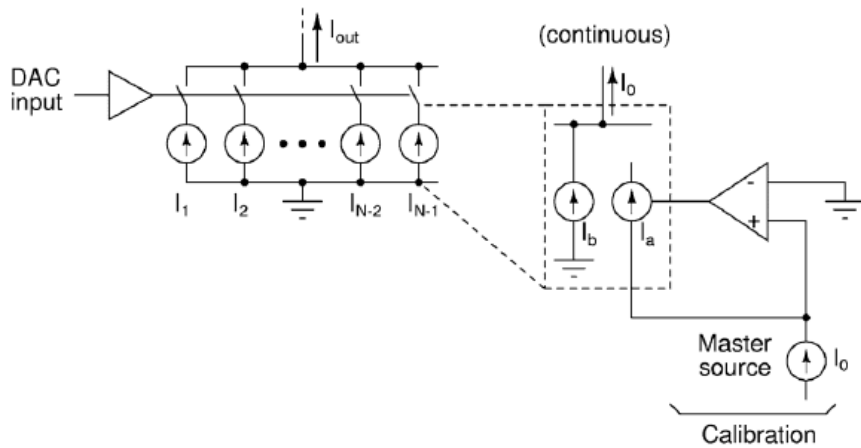

References

1. **Y. Chiu, *Data Converters Lecture Slides*, UT Dallas 2012.**
2. Rudy van de Plassche, “CMOS Integrated Analog-to-Digital and Digital-to-Analog Converters,” 2nd Ed., Springer, 2005..
3. B. Boser, *Analog-Digital Interface Circuits Lecture Slides*, UC Berkeley 2011.
 - D. K. Su and B. A. Wooley, JSSC, pp. 1224-1233, issue 12, 1993.
 - C.-H. Lin and K. Bult, JSSC, pp. 1948-1958, issue 12, 1998.
 - K. Khanoyan, F. Behbahani, A. A. Abidi, VLSI, 1999, pp. 73-76.
 - K. Falakshahi, C.-K. Yang, B. A. Wooley, JSSC, pp. 607-615, issue 5, 1999.
 - G. A. M. Van Der Plas et al., JSSC, pp. 1708-1718, issue 12, 1999.
 - A. R. Bugeja and B.-S. Song, JSSC, pp. 1719-1732, issue 12, 1999.
 - A. R. Bugeja and B.-S. Song, JSSC, pp. 1841-1852, issue 12, 2000.
 - A. van den Bosch et al., JSSC, pp. 315-324, issue 3, 2001.