

Part	Quant Description	Есть
Circuit board	1 β22 printed circuit board	1 оригинал
-		
Resistors		
R1	1 1/8W 1% metal film resistor 475Ω (see table below)	3 RN55D Vishay-Dale
R2	1 1/8W 1% metal film resistor 1MΩ (see table below)	3 RN55D Vishay-Dale
R2 Active Ground	1 1K	4 RN55D Vishay-Dale
R3	1 1/8W 1% metal film resistor 182Ω (see table below)	6 RN55D Vishay-Dale
R3 Gain 2	2.49KΩ	4 RN55D Vishay-Dale
R3 Active Ground	2.49KΩ	
R4	1 1/8W 1% metal film resistor 1.21KΩ (see table below)	5 RN55D Vishay-Dale
R4 Gain 2	1 2.49KΩ	4 RN55D Vishay-Dale
R4 Active Ground	1 2.49KΩ	
R5, R6	2 1/8W 1% metal-film resistor 49.9Ω	3 RN55D Vishay-Dale
R7, R8	2 1/8W 1% metal-film resistor 56.2Ω	3 RN55D Vishay-Dale
R9-R12, R25, R26	6 1/8W 1% metal-film resistor 2.21KΩ	4 RN55D Vishay-Dale
R13, RLED+, RLED-	3 1/8W 1% metal-film resistor 10KΩ	5 RN55D Vishay-Dale
R14, R15	2 1/8W 1% metal-film resistor 121Ω	3 RN55D Vishay-Dale
R16-R19	4 1/8W 1% metal-film resistor 10Ω	6 RN55D Vishay-Dale
R20, R21	2 1/8W 1% metal-film resistor 249Ω	3 RN55D Vishay-Dale
R22, R27	2 1/8W 1% metal-film resistor 562Ω	3 RN55D Vishay-Dale
R23, R24	2 1/8W 1% metal-film resistor 1.82KΩ	3 RN55D Vishay-Dale
R28, R29, R32	3 1/8W 1% metal-film resistor 75Ω	3 RN55D Vishay-Dale
R33	1 1/8W 1% metal-film resistor 33.2Ω	4 RN55D Vishay-Dale
R34, R35	2 2W 5% metal-oxide resistor 0.47Ω (see notes below)	10 XICON
Potentiometers		
VR1	1 3/8" multi-turn cermet trimpot 200Ω	
VR2	1 3/8" multi-turn cermet trimpot 500Ω	1 Bournce
VR3	1 3/8" multi-turn cermet trimpot 5KΩ	1 Bournce
Capacitors		
C1-C5	5 multilayer ceramic capacitor 33pF (see table below)	20 Murata NPO
C2-C5 Active Ground	4 100pF	8 Vishay
C2-C5 Gain 2	4 100pF	
C2-C5 Gain 5	4 47pF	20 Vishay
C6-C8, C13, C14, C17,	7 metallized polyester capacitor 1μF	1 Wima
C9-C12	4 aluminum electrolytic capacitor 100μF 50V	9 Panasonic EEUFC
C15, C16	2 aluminum electrolytic capacitor 470μF 50V	2 Nichicon
Transistors		
Q1, Q2	2 N-channel JFET 2SK170BL, 2SK370BL or LSK170B	2 Matched
Q3, Q4	2 P-channel JFET 2SJ74BL, 2SJ108BL or LSJ74B	2 Matched
Q5, Q6, Q11, Q12, Q1	8 NPN small signal BJT BC550C	10 измерены
Q7, Q8, Q9, Q10, Q13	8 PNP small signal BJT BC560C	9 измерены
Q19, Q20	2 N-channel JFET PN4392	8 измерены
Q21, Q23	2 International Rectifier N-channel power MOSFET IRFZ24N	5 измерены
Q22, Q24	2 International Rectifier P-channel power MOSFET IRF9Z34	6 измерены
Diodes		
D1, D2, D5-D10	8 12V 500mW zener diode BZX55C12	8 измерены
D3, D4	2 small signal diode 1N4148	9
D11, D12	2 1A rectifier diode 1N4004	8
CR1-CR8	8 Current regulator diode 0.5mA E-501	8 измерены